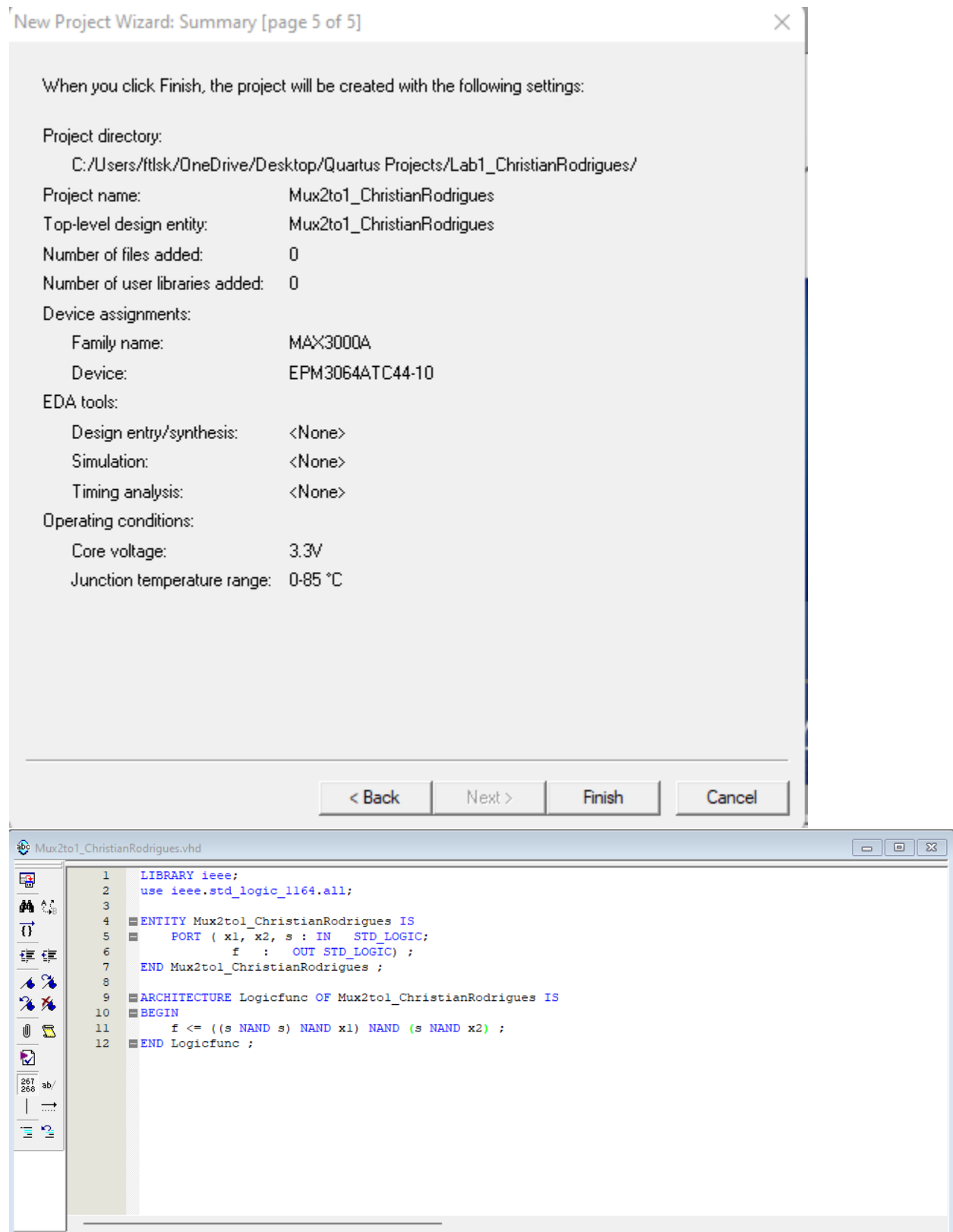




LAB1

The purpose of this lab is to create a 2 to 1 multiplexer and utilize it as a component to create a 4 to 1, 8 to 1, and 16 to 1 multiplexer.

Christian Rodrigues –
Petrie CDA3203 –
10/21/2022

2 to 1 Mux



 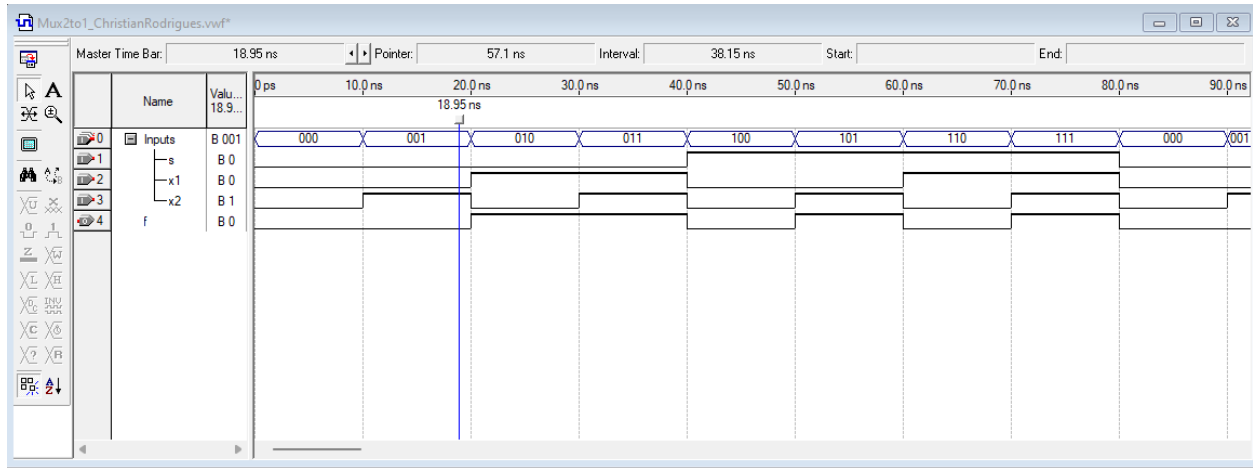

4 to 1 Mux

New Project Wizard: Summary [page 5 of 5] ✕

When you click Finish, the project will be created with the following settings:

Project directory:
C:/Users/ftlsk/OneDrive/Desktop/Quartus Projects/Lab1_ChristianRodrigues/



Project name: mux4to1_ChristianRodrigues
Top-level design entity: mux4to1_ChristianRodrigues
Number of files added: 1
Number of user libraries added: 0

Device assignments:
Family name: MAX3000A
Device: EPM3064ATC44-10

EDA tools:
Design entry/synthesis: <None>
Simulation: <None>
Timing analysis: <None>

Operating conditions:
Core voltage: 3.3V
Junction temperature range: 0-85 °C

 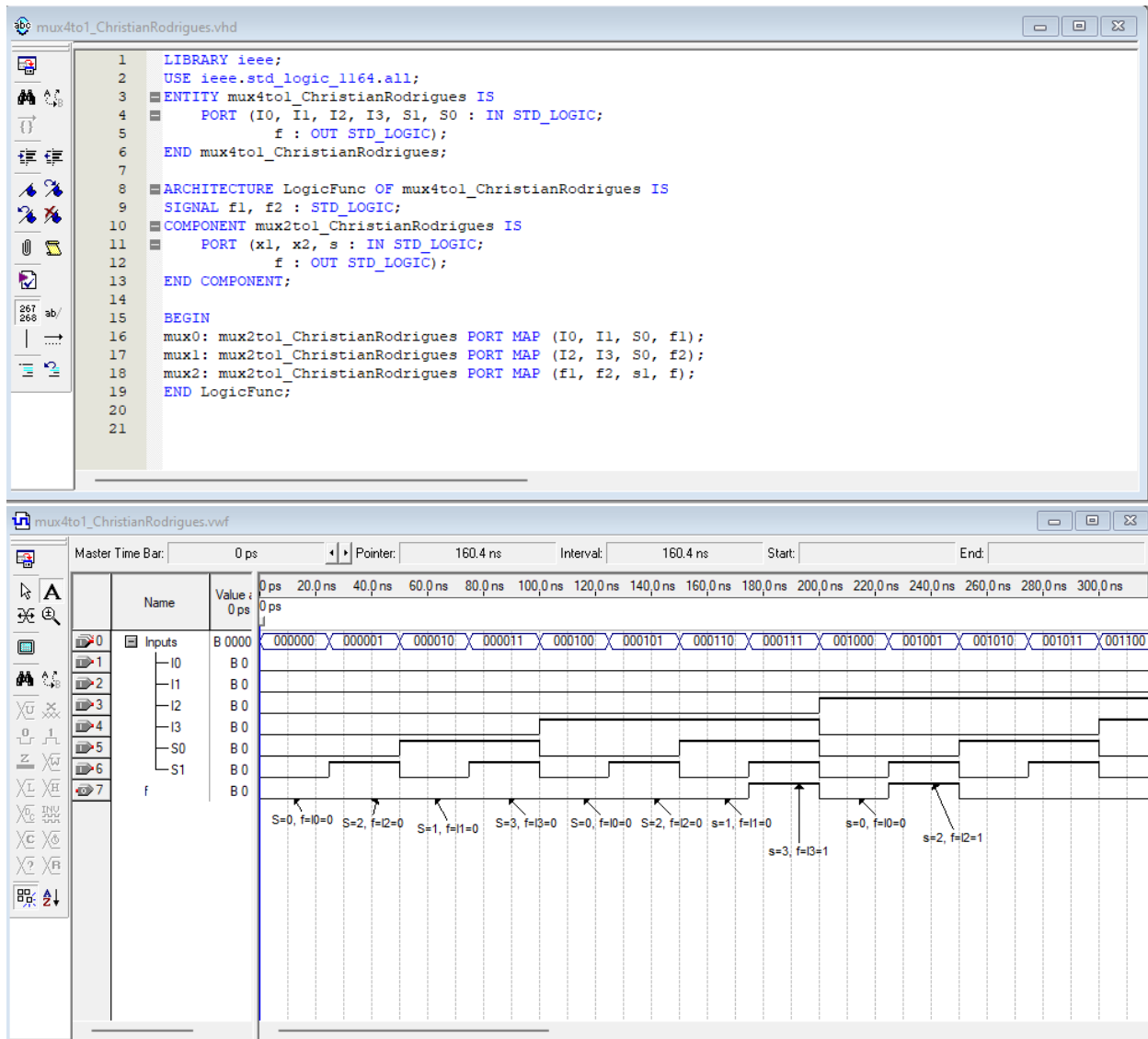[< Back](#) [Next >](#) [Finish](#) [Cancel](#)



8 to 1 Mux

New Project Wizard: Summary [page 5 of 5]



When you click Finish, the project will be created with the following settings:

Project directory:

C:/Users/ftlsk/OneDrive/Desktop/Quartus Projects/Lab1_ChristianRodrigues/

Project name: Mux8to1_ChristianRodrigues

Top-level design entity: Mux8to1_ChristianRodrigues

Number of files added: 2

Number of user libraries added: 0

Device assignments:

Family name: MAX3000A

Device: EPM3064ATC44-10

EDA tools:

Design entry/synthesis: <None>

Simulation: <None>

Timing analysis: <None>

Operating conditions:

Core voltage: 3.3V

Junction temperature range: 0-85 °C

< Back

Next >



Finish

Cancel

```

1  LIBRARY ieee;
2  use ieee.std_logic_1164.all;
3
4  ENTITY Mux8to1_ChristianRodrigues IS
5  PORT (I0, I1, I2, I3, I4, I5, I6, I7, S0, S1, S2 : IN STD_LOGIC;
6        f : OUT STD_LOGIC);
7  END Mux8to1_ChristianRodrigues;
8
9  ARCHITECTURE LogicFunc OF Mux8to1_ChristianRodrigues IS
10 COMPONENT mux4to1_ChristianRodrigues IS
11 PORT (I0, I1, I2, I3, S0, S1 : IN STD_LOGIC;
12       f : OUT STD_LOGIC);
13 END COMPONENT;
14
15 COMPONENT Mux2to1_ChristianRodrigues IS
16 PORT (x1, x2, s : IN STD_LOGIC;
17       f : OUT STD_LOGIC);
18 END COMPONENT;
19
20 SIGNAL f1, f2 : STD_LOGIC;
21 BEGIN
22 mux0: Mux4to1_ChristianRodrigues PORT MAP (I0, I1, I2, I3, S0, S1, f1);
23 mux1: Mux4to1_ChristianRodrigues PORT MAP (I4, I5, I6, I7, S0, S1, f2);
24 mux2: Mux2to1_ChristianRodrigues PORT MAP (f1, f2, S2, f);
25 END LogicFunc;

```

  

16 to 1 Mux

New Project Wizard: Summary [page 5 of 5]



When you click Finish, the project will be created with the following settings:

Project directory:

C:/Users/ftlsk/OneDrive/Desktop/Quartus Projects/Lab1_ChristianRodrigues/

Project name: Mux16to1_ChristianRodrigues

Top-level design entity: Mux16to1_ChristianRodrigues

Number of files added: 3

Number of user libraries added: 0

Device assignments:

Family name: MAX3000A

Device: EPM3064ATC44-10

EDA tools:

Design entry/synthesis: <None>

Simulation: <None>

Timing analysis: <None>

Operating conditions:

Core voltage: 3.3V

Junction temperature range: 0-85 °C

< Back

Next >



Finish

Cancel


```

1  LIBRARY ieee;
2  use ieee.std_logic_1164.all;
3
4  ENTITY Mux16to1_ChristianRodrigues IS
5  PORT (I0, I1, I2, I3, I4, I5, I6, I7, I8, I9, IA, IB, IC, ID, IE, INF, S0, S1, S2 : IN STD_LOGIC;
6        f : OUT STD_LOGIC);
7  END Mux16to1_ChristianRodrigues;
8
9  ARCHITECTURE LogicFunc OF Mux16to1_ChristianRodrigues IS
10 COMPONENT Mux8to1_ChristianRodrigues IS
11 PORT (I0, I1, I2, I3, I4, I5, I6, I7, S0, S1, S2 : IN STD_LOGIC;
12       f : OUT STD_LOGIC);
13 END COMPONENT;
14
15 COMPONENT Mux2to1_ChristianRodrigues IS
16 PORT (x1, x2, s : IN STD_LOGIC;
17       f : OUT STD_LOGIC);
18 END COMPONENT;
19
20 SIGNAL f1, f2 : STD_LOGIC;
21
22 BEGIN
23 mux0: Mux8to1_ChristianRodrigues PORT MAP (I0, I1, I2, I3, I4, I5, I6, I7, S0, S1, S2, f1);
24 mux1: Mux8to1_ChristianRodrigues PORT MAP (I8, I9, IA, IB, IC, ID, IE, INF, S0, S1, S2, f2);
25 mux2: Mux2to1_ChristianRodrigues PORT MAP (f1, f2, S2, f);
26 END LogicFunc;

```

 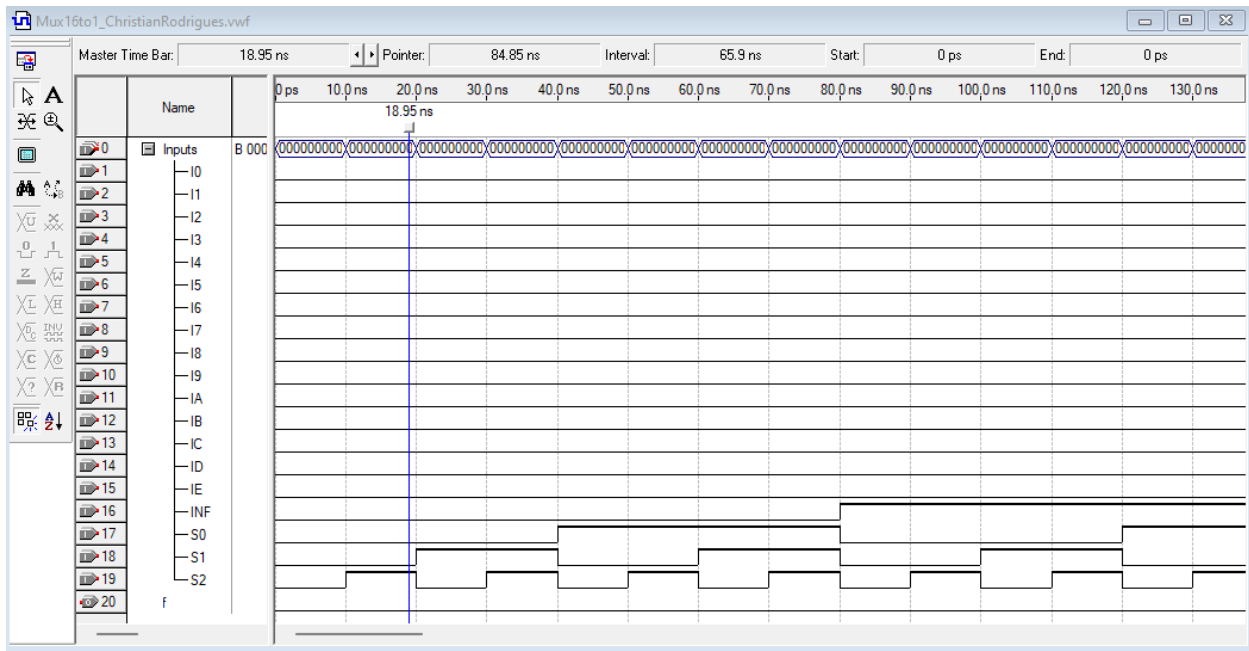

Lab 1: The objectives of this lab are:

- 1) Design circuit equivalents for all the logic gates using NOT-AND-OR gates and design equivalent circuits using only one of the universal gates: NAND or NOR. We will design all-NAND equivalent circuits.
- 2) Design the circuit using Altera Quartus II 9.1 Web Edition, and verify the circuit is correct by comparing the Timing Diagram results to the Truth Table of the circuit.
- 3) Design and simulate an Active-Low Decoder, (DMux) circuit.
- 4) Design and simulate a Multiplexer (Mux) circuit.

Part 1.

HANDWORK:

1. [40 pts.] Design 9 circuits by completing below: Draw the symbol for the gate, its Truth Table, its Simplest Sum of Products Expression, draw its NOT-AND-OR Equivalent Circuit, its all-NAND Equivalent Circuit.




1.1 Draw NOT gate:

Truth Table:

A	NOT(A)
0	1
1	0

NOT-AND-OR Equivalent Circuit

all-NAND Equivalent Circuit:

   

$$Y1 = A'$$




1.2 Draw AND gate:

Truth Table:

A	B	AND(A,B)
0	0	0
0	1	0
1	0	0
1	1	1

NOT-AND-OR Equivalent Circuit

all-NAND Equivalent Circuit:

   

$$Y2 = AB$$



1.3 Draw OR gate:

Truth Table:

A	B	OR(A,B)
0	0	0
0	1	1
1	0	1
1	1	1

NOT-AND-OR Equivalent Circuit

all-NAND Equivalent Circuit:

  

$$Y3 = A + B$$




1.4 Draw XOR gate:

Truth Table:

A	B	XOR(A,B)
0	0	0
0	1	1
1	0	1
1	1	0

NOT-AND-OR Equivalent Circuit

all-NAND Equivalent Circuit:

   


$$Y4 = A \oplus B$$

1.5 Draw NAND gate:



Truth Table:

A	B	NAND(A,B)
0	0	1
0	1	1
1	0	1
1	1	0

 

$$Y5 = A'B'$$

  
NOT-AND-OR Equivalent Circuit: all-NAND Equivalent Circuit:



1.6 Draw NOR gate:



Truth Table:

A	B	NOR(A,B)
0	0	1
0	1	0
1	0	0
1	1	0

 

$$Y6 = A' + B'$$

  
NOT-AND-OR Equivalent Circuit: all-NAND Equivalent Circuit:



1.7 Draw XNOR gate:



Truth Table:

A	B	XNOR(A,B)
0	0	1
0	1	0
1	0	0
1	1	1

 

$$Y7 = A \oplus B'$$

 
 
NOT-AND-OR Equivalent Circuit: all-NAND Equivalent Circuit:



1.8 2-to-1 Encoder or Multiplexer (Mux):

Truth Table:

s	X ₁	X ₀	mux
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

  

$$Y8 = sX_1 + sX_0$$

1.9 Draw 2-to-4-Decoder Truth Table: NOT-AND-OR Equivalent Circuit:

all-NAND Equivalent Circuit:

X ₁	X ₀	F ₃	F ₂	F ₁	F ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$Y9 =$$

